 


Q. 1 Choose the correct answer.**[03]**

- (1) The field effect transistor (FET) is a _____ operated devices.
(A) Voltage (C) Resistance
(B) Current (D) None of above
- (2) Unit of light intensity is _____.
(A) Lumens (C) Volts
(B) Ampere (D) None of above
- (3) Potential divider Bias circuit in FET is _____ biasing circuit.
(A) Best (C) Worst
(B) Not good (D) None of above

**Q.2 Answer the following in short.(Attempt any two, each two marks)****[04]**

- (1) Draw the diagram showing construction and cross section of solar cell.
- (2) List different FET parameters and explain any one in brief.
- (3) Draw a neat potential divider bias circuit using n-channel FET.

Q.3 Draw a frequency response for transistor amplifier and explain why gain of amplifier falls off at lower frequency end. **[06]**

OR

Q.3 Explain principle and construction of n-channel JFET and draw the drain characteristics for n-channel JFET and label it. **[06]**

Q.4 Explain construction and working of n-channel enhancement MOSFET, also draw the diagram showing construction of n-channel enhancement-depletion MOSFET. **[06]**

OR

Q.4 Give an account of self bias FET circuit. **[06]**

Q.5 Give an account of photomultiplier tube. **[06]**

OR

Q. 5 Give an account of LCD (liquid crystal display). **[06]**