

V.P & R.P.T.P. SCIENCE, V.V.NAGAR

B.Sc. (Vth SEM.) ELECTRONICS Internal Exam

DATE: 06/10/2018

SUB: US05CELE05

TIME: 10:00 am to 12:00 noon

MARKS-50

Q-1 Choose correct answer [08]

1. Thyristor mainly used for _____.
(A) Power controlling (C) Relaxation oscillation
(B) Rectification (D) None of above
2. Recommended method to TURN-ON SCR is _____.
(A) Triggering by A.C signal (C) Triggering by D.C signal
(B) Triggering by pulse signal (D) None of above
3. Dc motor consists of _____.
(A) TRIAC (C) Amplifier
(B) Stator (D) None of above
4. Stepper motor used for _____ speed variation.
(A) Discrete (C) Linear
(B) Constant (D) None of above
5. UJT mainly used for _____.
(A) relaxation oscillator (C) amplification
(B) rectification (D) None of above
6. TRIAC _____ type of device.
(A) multi-directional (C) bi-directional
(B) uni-directional (D) None of above
7. _____ Connection of SCR used for controlling very high current.
(A) series (C) bi-directional
(B) parallel (D) None of above
8. _____ is a circuit which convert DC power in to AC power at desired output voltage.
(A) Rectifier (C) Filter
(B) Inverter (D) None of above



Q-2 Short answer type question. (any Five) [10]

1. Define string efficiency.
2. State function of gate in SCR.
3. Differentiate between semiconductor and thyristor device.
4. Differentiate between D.C. motor and stepper motor.
5. Define reverse recovery current I_{RR} .
6. List application of thyristor device.
7. Differentiate TRIAC and SCR.
8. State different type of inverter circuit.

Q.3 List the thyristor family components and Discuss principle of operation and characteristics of SCR. [08]

OR

Q.3 Explain different method of turning on a SCR with TURN-ON characteristics. [08]

Q.4 Discuss the series operation of SCR with necessary diagram and compensation circuits. [08]

OR

Q.4 Discuss the parallel operation of SCR with necessary diagram and compensation circuits. [08]

Q.5 Discuss characteristics and operation of UJT with necessary diagram. [08]

OR

Q.5 Discuss different triggering modes of TRIAC. [08]

Q.6 Draw the schematic diagram of D.C motor and discuss its working in detail. [08]

OR

Q.6 (a) Explain series inverter giving necessary diagram and waveforms. [05]

Q.6 (b) Write a brief note on stepper motor [03]